

#### BIOMEDICAL INSTRUMENTATION

# ECG Amplifier Laboration

Authors: Courtney Keeler Arsalan Latif  $\begin{array}{c} \textit{Professor:} \\ \text{Dr. Sabine Reinfeldt} \\ \textit{TA:} \\ \text{Cristina Rigato} \end{array}$ 

#### 1 Introduction

Electrocardiography (ECG) amplifiers are common medical devices that are used to measure the electrical activity of a patient's heart. The body surface potentials that are physically measured by the device are very small in amplitude, and therefore require an amplifier that attenuates noise while amplifying the desired signal, all while protecting both the patient and the instrument. In this lab, an ECG amplifier circuit was analyzed, built, and verified on a patient in the lab.

#### 2 Design and Simulation

The basic requirements for ECG circuitry are high input impedance, high gain for the desired frequency range, and high common mode rejection ratio (CMRR). These parameters are set by the circuit designer through choice of component values. The overall schematic of the ECG amplifier circuit is shown in Figure 1.

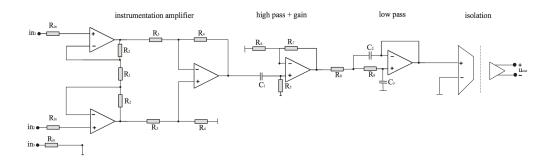


Figure 1: Schematic of the circuitry used to amplify ECG signals in the laboratory.

High input impedance but we use 100k because else the signal disappears

#### 2.1 AC Analysis


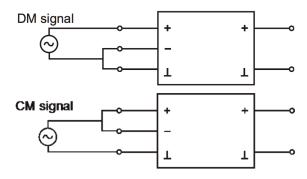
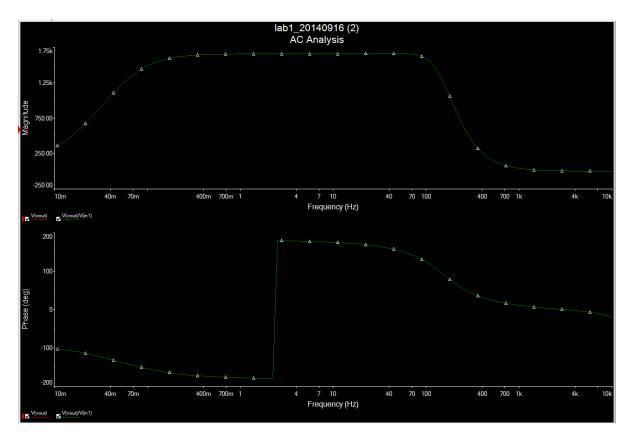



Figure 2: Schematic of the input configurations for measuring DM and CM signals.

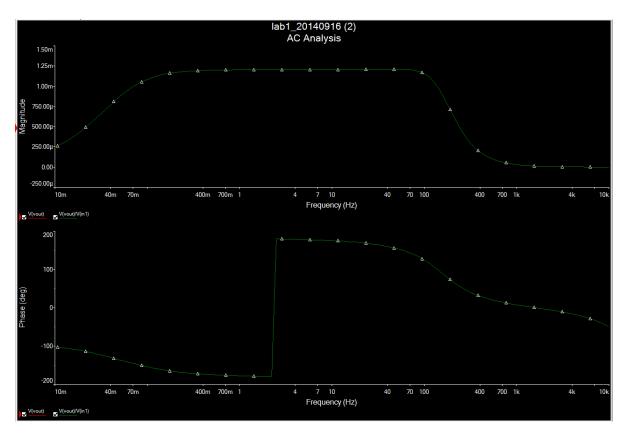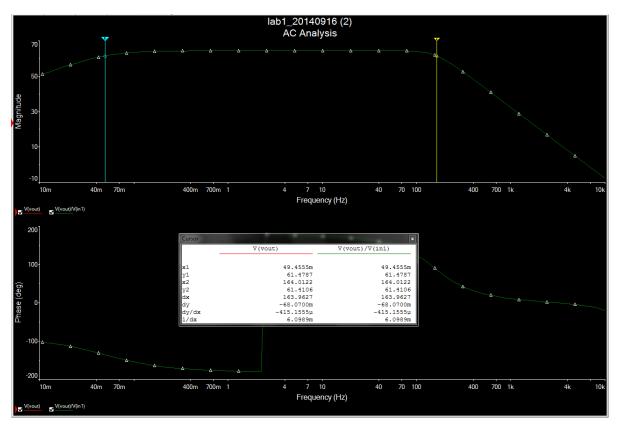

**Figure 3:** AC analysis of the simulated ECG amplifier circuit in DM measurement configuration.

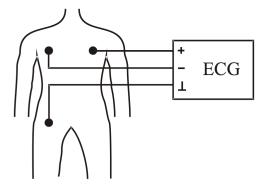


**Figure 4:** AC analysis of the simulated ECG amplifier circuit in CM measurement configuration.




**Figure 5:** AC analysis of the simulated ECG amplifier circuit in CM measurement configuration. The y-axis is plotted in decibels in order to easily find the -3dB cutoff frequencies.

## 3 Construction and Data Acquisition



**Figure 6:** Schematic of the electrode placement for the acquisition of ECG signals in the laboratory.

## 4 Results

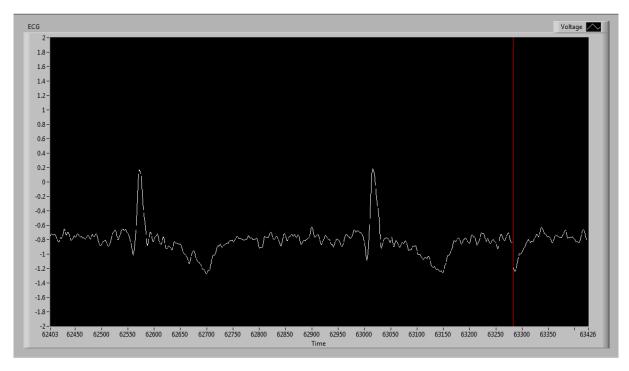

**Figure 7:** Captured waveform from the ECG amplifier circuit when hooked up to electrodes placed on a patient.

#### 5 Device Limitations

#### References

[1] Webster, John G. Medical Instrumentation Application and Design, 4th Edition. John Wiley & Sons, 092008. VitalBook file.